
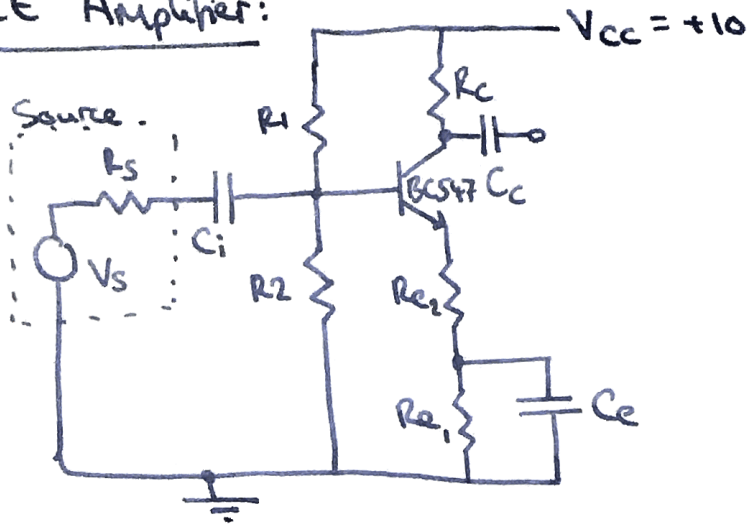


CE Amplifier:

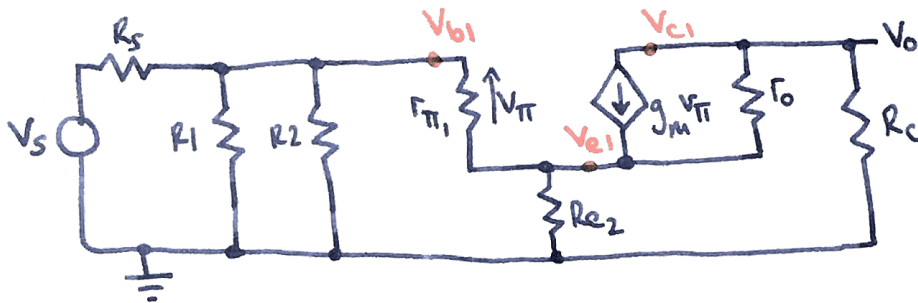

Small Signal Model: (capacitors become short circuits).



$$V_e = \left(g_m v_{\pi} + \frac{V_{be}}{r_{\pi 1}} \right) R_{E2}$$

$$= v_{\pi} \left(g_m + \frac{1}{r_{\pi 1}} \right) R_{E2}$$

$$= v_{\pi} (g_m + g_{\pi}) R_{E2}$$

$$\left. \begin{array}{l} \\ \end{array} \right\} \text{let } \frac{1}{r_{\pi 1}} = g_{\pi}$$

$$\therefore V_e = v_{\pi} R_{E2} (g_m + g_{\pi})$$

$$V_{in} = v_{\pi} + V_e$$

$$= v_{\pi} + v_{\pi} (g_m + g_{\pi}) R_{E2}$$

$$\therefore v_{\pi} = \frac{V_{in}}{1 + (g_m + g_{\pi}) R_{E2}}$$

$$V_o = \frac{-g_m R_C V_{in}}{1 + (g_m + g_{\pi}) R_{E2}}$$

$$\text{As } \frac{V_{in}}{1 + (g_m + g_{\pi}) R_{E2}} = v_{\pi}$$

$$\therefore V_o = -g_m V_{\pi} R_c$$

$$\frac{V_o}{V_{in}} = \text{Gain} = \frac{-g_m R_c}{1 + (g_m + g_{\pi}) R_c}$$

but we said $g_{\pi} = \frac{1}{r_{\pi 1}}$

also $r_{\pi 1} = \frac{\beta}{g_m}$

$$\therefore \frac{V_o}{V_{in}} = \frac{-g_m R_c}{1 + (g_m + \frac{1}{r_{\pi 1}}) R_c}$$

$$= \frac{-g_m R_c}{1 + R_c (g_m + \frac{g_m}{\beta})}$$

$$= \frac{-g_m R_c}{1 + g_m R_c (1 + \frac{1}{\beta})}$$

$$= \frac{-g_m \beta R_c}{\beta + g_m R_c (\beta + 1)}$$

as $\beta = g_m r_{\pi}$ cancel g_m

$$= \frac{-\beta R_c}{r_{\pi 1} + R_c (\beta + 1)}$$

$$\therefore \frac{V_o}{V_{in}} = \frac{-\beta R_c}{r_{\pi 1} + R_c (\beta + 1)} = \text{Gain of CE Amplifier.}$$


CE Amplifier Input Impedance:

$$\begin{aligned}\text{Resistance at base terminal: } R_b &= \frac{V_{b1}}{I_{b1}} = \frac{V_{b1}}{(V_{b1} - V_{e1}) / r_{\pi 1}} \\ &= \frac{r_{\pi 1}}{1 - \frac{V_{e1}}{V_{b1}}} \\ &= r_{\pi 1} \left(1 + g_m R_{e2} \left(1 + \frac{1}{\beta} \right) \right)\end{aligned}$$

$$\text{As } g_m r_{\pi 1} = \beta$$

$$\begin{aligned}\therefore R_b &= r_{\pi} + \beta R_{e2} \left(1 + \frac{1}{\beta} \right) \\ &= r_{\pi} + R_{e2} (\beta + 1)\end{aligned}$$

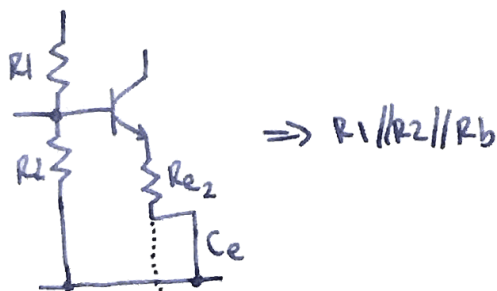Input impedance R_{in} is given by the parallel combination of R_1 , R_2 and R_b



$$\therefore R_{in1} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_b} \right)^{-1}$$


$$R_{in} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{r_{\pi} + R_{e2} (\beta + 1)} \right)^{-1}$$

Output Impedance of CE Amplifier:


Simply the parallel combination $R_c // R_L$ where R_L is the load on the amplifier

$$R_o = \left(\frac{1}{R_c} + \frac{1}{R_L} \right)^{-1}$$


CC Amplifier:

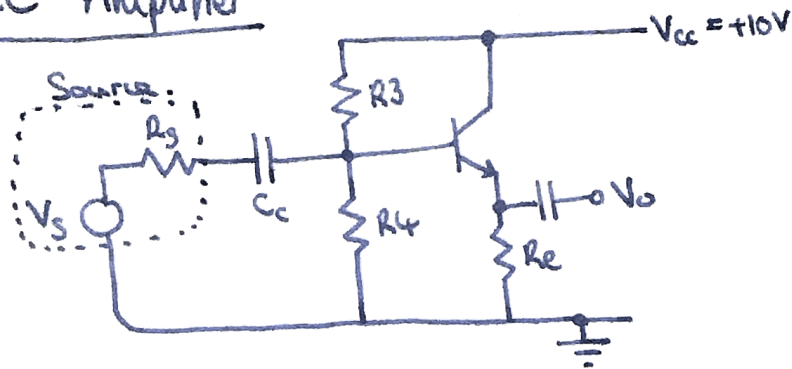

Small Signal Equivalent:

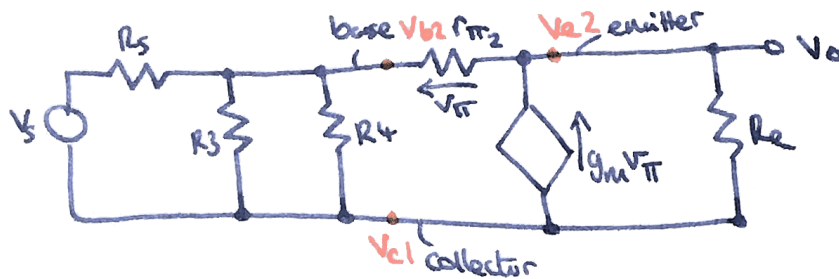

Ignore R3, R4, Rs for gain calculation:

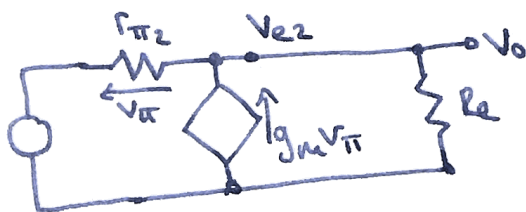

Applying KCL at V_{e2} - emitter node:

$$g_m(V_e - V_s) + \frac{V_e - V_s}{r_{\pi 2}} + \frac{V_e}{R_e} = 0$$

$$\text{using } g_m = \frac{\beta}{r_{\pi 2}}$$

$$\frac{\beta}{r_{\pi 2}}(V_e - V_s) + \frac{V_e - V_s}{r_{\pi 2}} + \frac{V_e}{R_e} = 0$$

$$\beta V_e - \beta V_s + V_e - V_s + \frac{V_e r_{\pi 2}}{R_e} = 0$$

$$V_e \left(1 + \beta + \frac{r_{\pi 2}}{R_e} \right) - V_s (1 + \beta) = 0$$

$$\frac{V_e}{V_s} = \frac{1 + \beta}{1 + \beta + \frac{r_{\pi 2}}{R_e}} = \frac{R_e (1 + \beta)}{R_e (1 + \beta) + r_{\pi 2}} = \text{Gain}$$

No voltage gain!

CC Amplifier Input Impedance:

By examining the input current:

$$\begin{aligned} i_{b2} &= \frac{V_s - V_{e2}}{r_{\pi 2}} = \frac{V_s}{r_{\pi 2}} - \frac{V_{e2}}{r_{\pi 2}} \quad \begin{array}{l} \swarrow \text{from our gain equation} \\ \text{we can put this in} \\ \text{terms of } V_s \end{array} \\ &= \frac{V_s}{r_{\pi 2}} - \frac{V_s}{r_{\pi 2}} \left(\frac{R_e(1+\beta)}{R_e(1+\beta) + r_{\pi 2}} \right) \\ &= \frac{V_s}{r_{\pi 2}} \left(1 - \frac{R_e(1+\beta)}{R_e(1+\beta) + r_{\pi 2}} \right) \\ &= \frac{V_s}{r_{\pi 2} + R_e(1+\beta)} \end{aligned}$$

Resistance of base input:

$$R_{b2} = \frac{V_{s b2}}{i_{b2}} = \frac{V_s}{i_{b2}} = r_{\pi 2} + R_e(1+\beta)$$

Resistance at input to amplifier has a source resistance as well.


$$\therefore R_{in2} = R_{b2} \parallel R_s$$

$$R_{in2} = \left(\frac{1}{R_s} + \frac{1}{r_{\pi 2} + R_e(1+\beta)} \right)^{-1}$$

n.b. R_s is also in parallel with R_3 and R_4 but dominates the resistance. i.e. $R_s \parallel R_3 \parallel R_4 \approx R_s$

CC Amplifier Output Impedance:

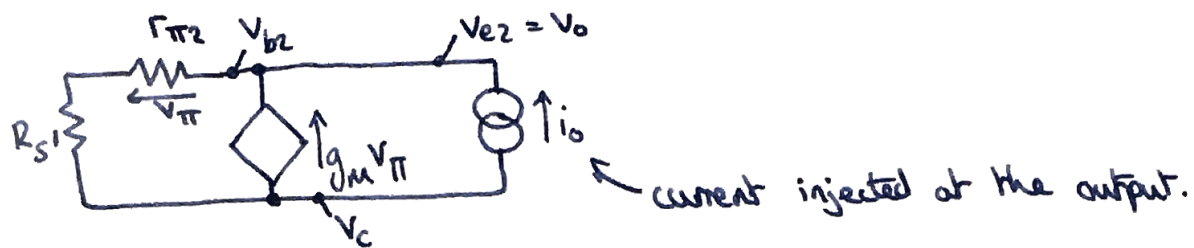By small signal analysis we get this model:



$R_{S'}$ is the effective source resistance $R_S // R_3 // R_4$

Applying KCL:

$$\textcircled{1} \quad i_o + g_m V_{\pi} - \frac{V_o}{R_{S'} + r_{\pi2}} = 0$$

$$\textcircled{2} \quad V_{\pi} = - \frac{V_o r_{\pi2}}{R_{S'} + r_{\pi2}}$$

$$\begin{aligned} \text{from } \textcircled{1} \text{ \& } \textcircled{2}: \quad i_o &= V_o \left(\frac{g_m r_{\pi2}}{R_{S'} + r_{\pi2}} + \frac{1}{R_{S'} + r_{\pi2}} \right) \\ &= \frac{(1 + \beta) V_o}{R_{S'} + r_{\pi2}} \end{aligned}$$

$$\therefore R_{out2} = \frac{V_o}{i_o} = \frac{R_{S'} + r_{\pi2}}{1 + \beta}$$

Typically very low output impedance for a CC amplifier
↳ used as a buffer regularly as a result.